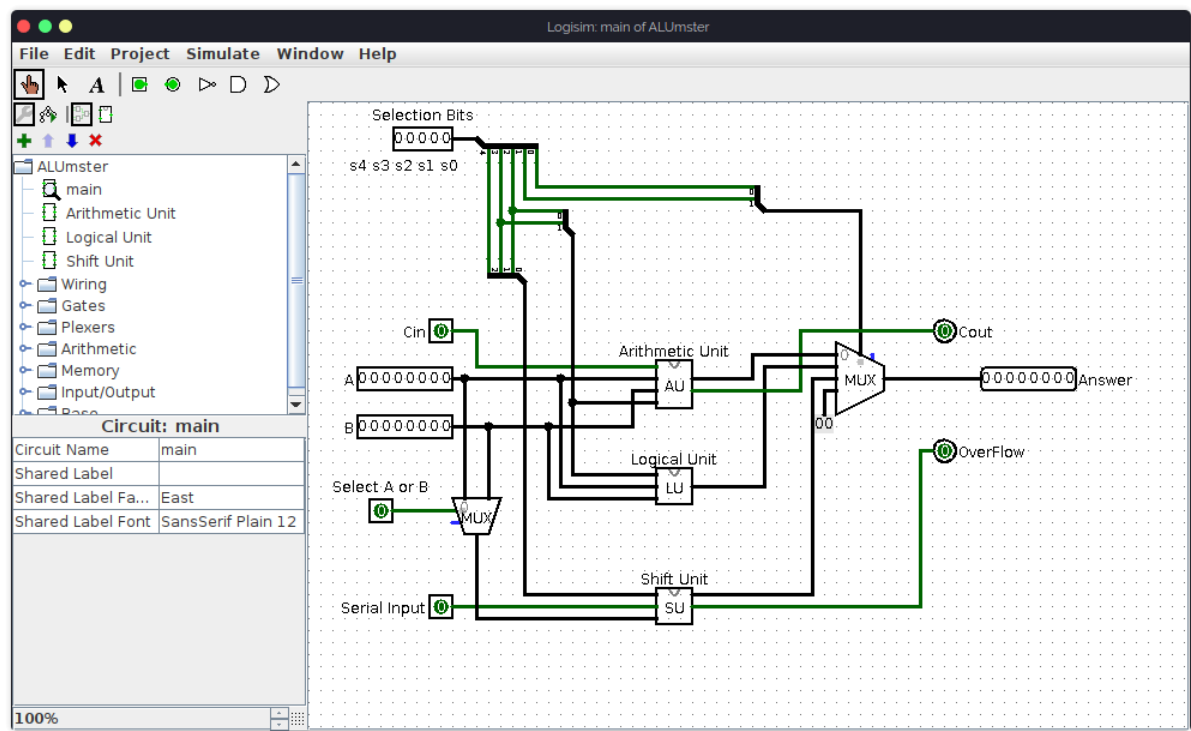


# Arithmetic, Logic and Shift Unit (ALSU) Report

Name: Shrey Viradiya

Roll No: 18BCE259

This is my arithmetic logic and shift unit implemented in the Logisim.



In this circuit we have two main inputs A & B, both are 8-bit long, five selection inputs S0 to S4, a Cin input, Select A or B for Shift Unit and Serial Input for Shift Unit. As output 8-bit output is answer and Cout and Overflow bit are provided.

## Selection Description:

Table 1: Selecting Unit

S1	S0	Description
0	0	Arithmetic Unit Activate
0	1	Logical Unit Activate
1	0	Shift Unit Activate

Table 2: Selecting Operation in Arithmetic Unit

S3	S2	Cin	Description
0	0	0	Add
0	0	1	Add with carry
0	1	0	Subtract with carry
0	1	1	Subtract
1	0	0	Transfer A
1	0	1	Increment A
1	1	0	Decrement A
1	1	1	Transfer A

Table 3: Selecting Operation in Logic Unit

S3	S2	Description
0	0	AND Operation
0	1	OR Operation
1	0	XOR Operation
1	1	NOT Operation

Table 4: Selecting Operation in Shift Unit

S4	S3	S2	Description
0	0	0	Logical Shift Left
0	0	1	Logical Shift Right
0	1	0	Circular Shift Left
0	1	1	Circular Shift Right
1	0	0	ArithmeticShift Left
1	0	1	ArithmeticShift Right

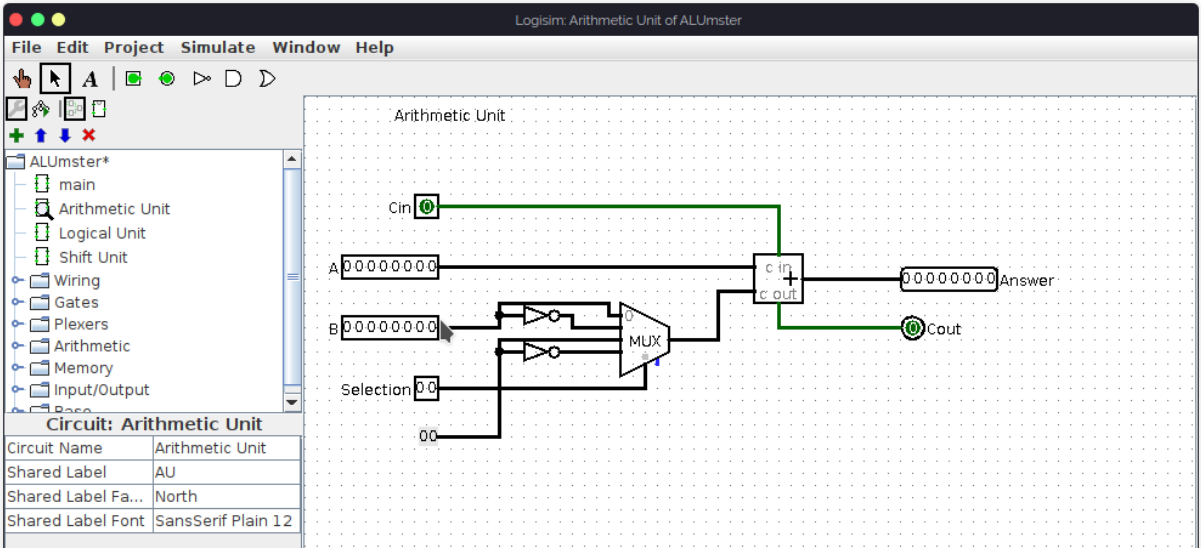


Image above is Screenshot of Arithmetic Unit. Along with inputs of A & B, Selection bits S2, S3 and Cin are inputs of this sub circuit. S2, S3 and Cin decides operation according to the table 2 above. Output of this circuit is handled by main circuit.

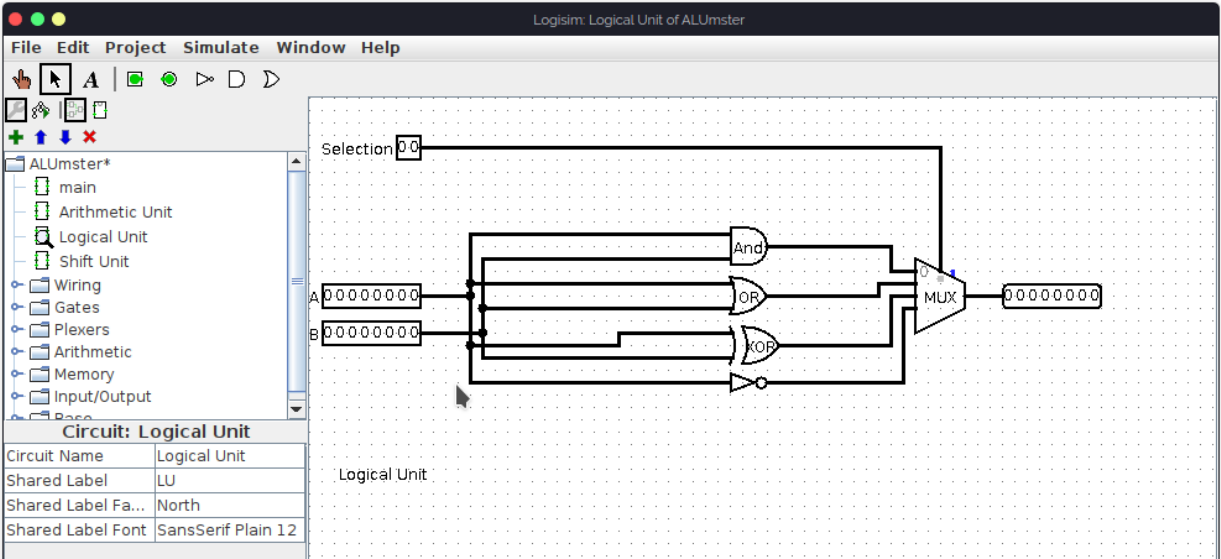


Image above is screenshot of Logical Unit. Here A, B and S2, S3 selection bits are input. Output is logical operation between A and B according to the selection S2, S3. Refer table 3.

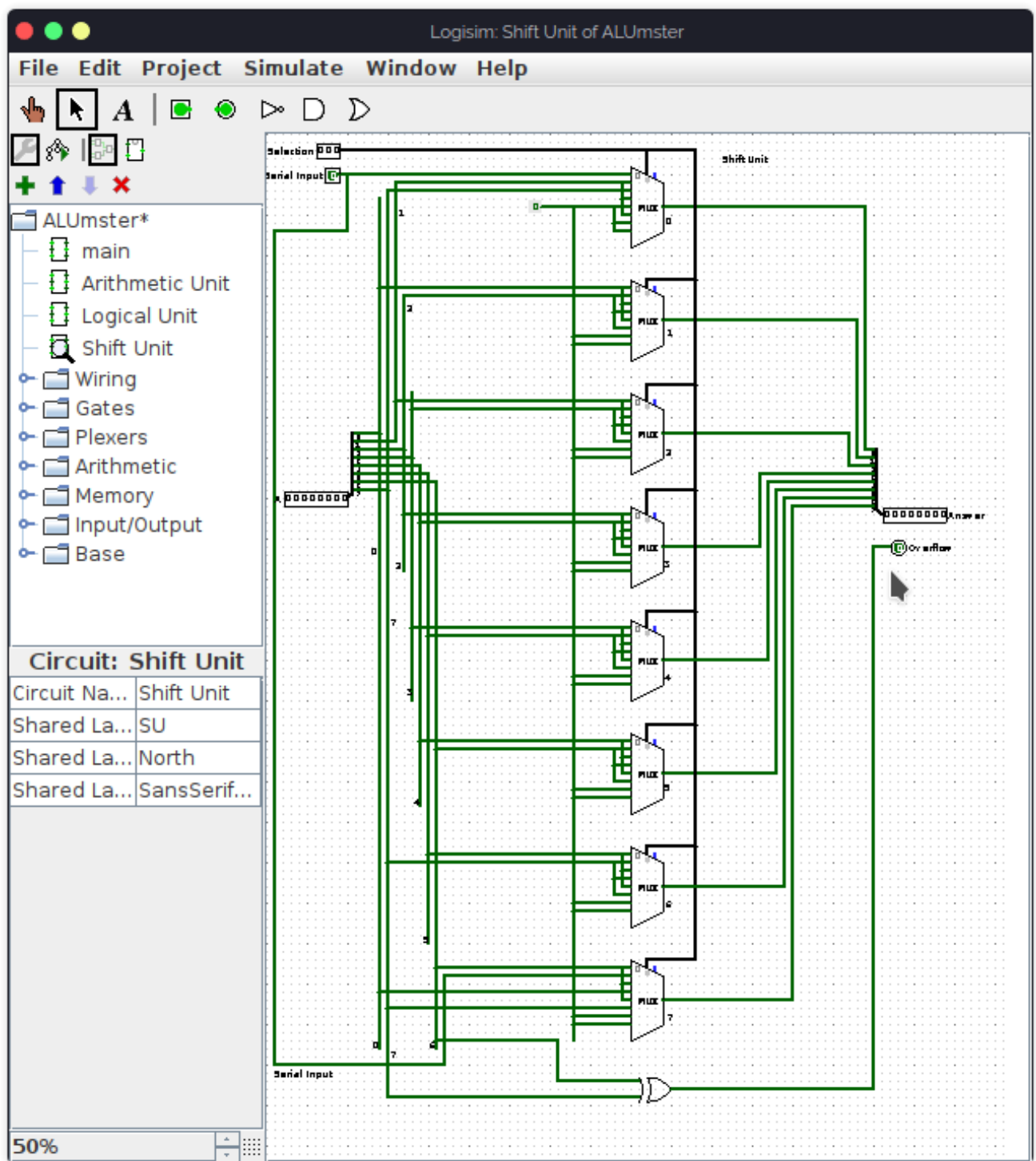


Image above is screenshot of shift unit. Selection of A or B will be done in main circuit. After selection input will be fed to this shift unit along with serial input and S4, S3, S2 selection inputs. Output will be given. Refer Table 4

With these outputs of 3 Units, multiplexer in the main circuit will give output according to the S0 and S1. Refer Table 1